

Cathodyne or Concertina Phase Splitter (CPS) Derivations

Fix-biased version

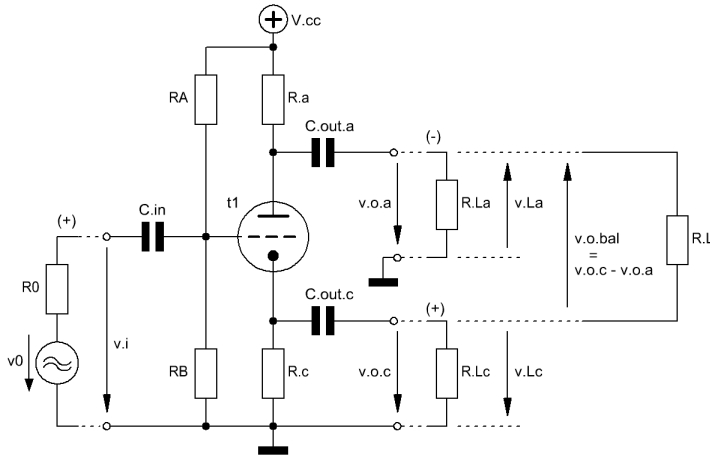


Fig. 10.1a Basic CPS circuit with fixed bias

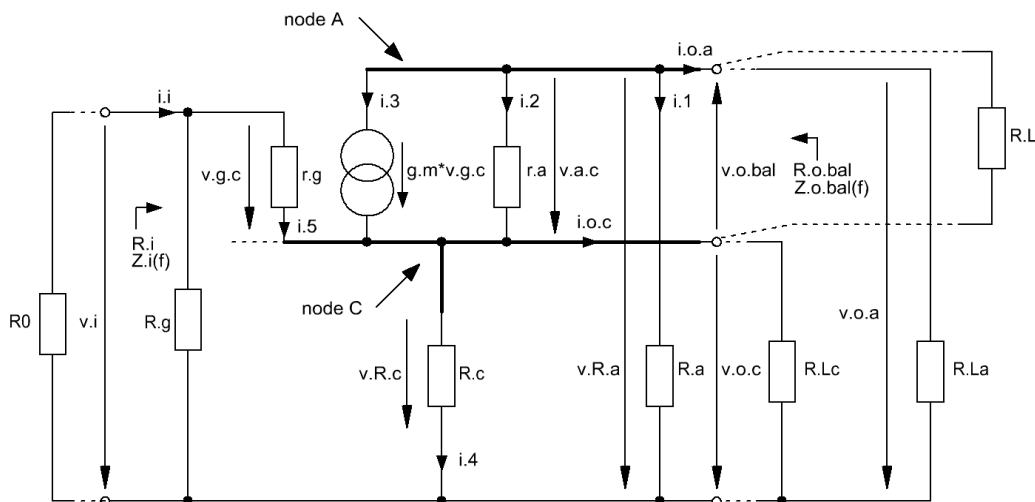


Fig. 10.7a Equivalent circuit of Fig. 10.1a

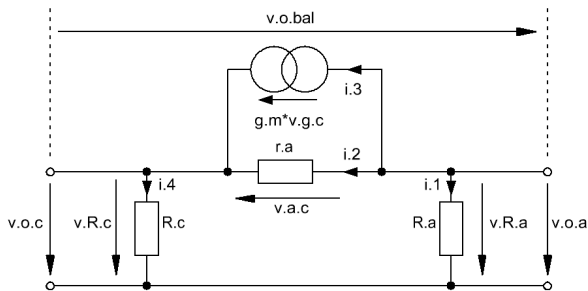


Fig. 10.8a Stripped down equivalent circuit

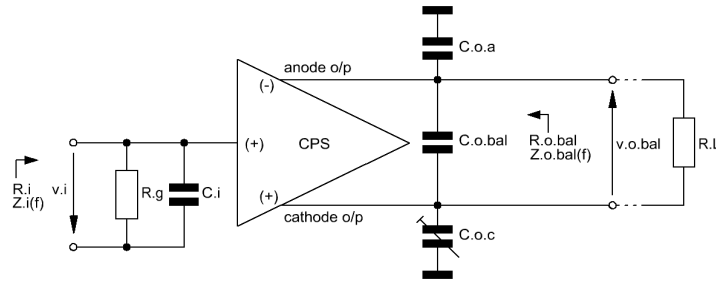


Fig. 10.9 Un-balanced to balanced conversion

Circuit variables à la S. Y.

$$g_m := 7.2 \cdot 10^{-3} \text{ S} \quad \mu := 31 \quad r_a := \frac{\mu}{g_m} \quad r_a = 4.306 \times 10^3 \Omega$$

$$R_{c1} := 1.4 \cdot 10^3 \Omega \quad R_c := 15 \cdot 10^3 \Omega \quad R_a := 15 \cdot 10^3 \Omega \quad V_g := -1.73 \text{ V}$$

$$I_a := 5.4 \cdot 10^{-3} \text{ A} \quad V_a := 88 \text{ V} \quad V_{cc} := V_a + I_a \cdot (R_a + R_c) \quad V_{cc} = 250 \text{ V}$$

$$R_A := 2.21 \cdot 10^6 \Omega \quad R_B := R_A \cdot \left( \frac{V_{cc} - I_a \cdot R_c - V_a + |V_g|}{V_{cc} - I_a \cdot R_c - |V_g|} \right) \quad R_B = 1.093 \times 10^6 \Omega$$

$$R_g := \left( \frac{1}{R_A} + \frac{1}{R_B} \right)^{-1} \quad R_g = 731.333 \times 10^3 \Omega \quad V_{cc} - I_a \cdot R_c - V_a + |V_g| = 82.73 \text{ V}$$

$$V_{cc} - I_a \cdot R_c - |V_g| = 167.27 \text{ V}$$

1. CPS used as un-balanced to balanced converter

1.1 Gains

1.1.1 Idle gains  $G_0$

cathode gain  $G_c$

$$G_{0,c} := \mu \cdot \frac{R_c}{r_a + R_a + (1 + \mu) \cdot R_c} \quad G_{0,c} = 931.293 \times 10^{-3}$$

anode gain  $G_a$

$$G_{0,a} := -\mu \cdot \frac{R_a}{r_a + R_a + (1 + \mu) \cdot R_c} \quad G_{0,a} = -931.293 \times 10^{-3}$$

equal loads R lead to the general idle gain equation  $G_0$  and  $G_{0,bal}$

$$R_a = R_c = R \quad \Rightarrow \quad |G_{0,a}| = G_{0,c} = G_0 = \mu \cdot \frac{R}{r_a + (2 + \mu) \cdot R}$$

$$v_{o,bal} = v_{o,c} - v_{o,a} \quad v_{o,c} = G_{0,c} \cdot v_i \quad v_{o,a} = G_{0,a} \cdot v_i$$



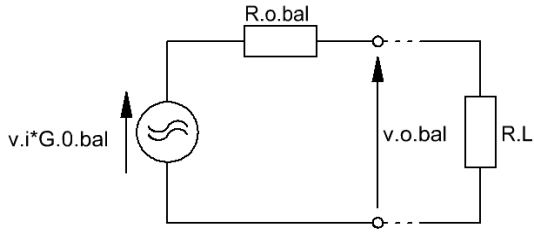


Fig. 10.10 Equivalent circuit of the balanced situation

$$v_{o.bal} = v_i \cdot G_{0.bal} \cdot \frac{R_L}{R_{o.bal} + R_L} \quad \frac{v_{o.bal}}{v_i} = G_{bal}(R_L) \Rightarrow G_{bal}(R_L) = G_{0.bal} \cdot \frac{R_L}{R_{o.bal} + R_L}$$

$$\Rightarrow R_{o.bal1} := \frac{G_{0.bal} \cdot R_L - G_{bal}(R_L) \cdot R_L}{G_{bal}(R_L)}$$

$$R_{o.bal1} = 258.693 \times 10^0 \Omega$$

$$R_{o.bal2} := R_L \cdot \left( \frac{G_{0.bal}}{G_{bal}(R_L)} - 1 \right)$$

$$R_{o.bal2} = 258.693 \times 10^0 \Omega$$

Simplification of the  $R_{o.bal}$  equation

$$\left[ \frac{\frac{2 \cdot \mu \cdot R}{r_a + (2 + \mu) \cdot R} \cdot R_L - R_L}{2 \cdot \mu \cdot \left( \frac{1}{R} + \frac{1}{0.5 \cdot R_L} \right)^{-1}} \cdot R_L - R_L \right] = 258.693 \times 10^0 \Omega$$

$$\Rightarrow R_{o.bal} := \frac{2 \cdot r_a \cdot R}{r_a + (\mu + 2) \cdot R}$$

$$R_{o.bal} = 258.693 \times 10^0 \Omega$$

### 1.3 Input and Output Capacitances

$C_a$  and  $C_{o.bal}$  plus trimming of  $C_{o.c}$  will lead to frequency dependent  $G_{bal}(f)$  and o/p impedance  $Z_{o.bal}(f)$  as follows:

$$f := 10\text{Hz}, 20\text{Hz}.. 10^5\text{Hz}$$

$$C_{g.c} := 3.1 \cdot 10^{-12}\text{F}$$

$$C_{g.a} := 1.4 \cdot 10^{-12}\text{F}$$

$$C_{a.c} := 3.0 \cdot 10^{-12}\text{F}$$

$$C_{o.bal} := C_{a.c}$$

$$Z_{o.bal}(f) := \left( \frac{1}{R_{o.bal}} + 2j \cdot \pi \cdot f \cdot C_{o.bal} \right)^{-1}$$

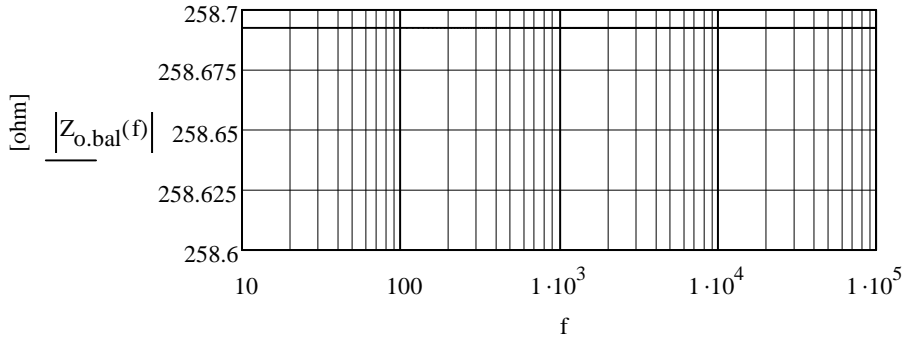


Fig. 10.11 Output impedance vs. frequency

$$G_a(R_L) := \frac{-\mu \cdot \left( \frac{1}{R} + \frac{1}{0.5 \cdot R_L} \right)^{-1}}{r_a + (2 + \mu) \cdot \left( \frac{1}{R} + \frac{1}{0.5 \cdot R_L} \right)^{-1}}$$

$$G_c(R_L) := \frac{\mu \cdot \left( \frac{1}{R} + \frac{1}{0.5 \cdot R_L} \right)^{-1}}{r_a + (2 + \mu) \cdot \left( \frac{1}{R} + \frac{1}{0.5 \cdot R_L} \right)^{-1}}$$

$$C_i := C_{g.a} \cdot (1 - G_a(R_L)) + C_{g.c} \cdot (1 - G_c(R_L))$$

$$C_i = 2.957 \times 10^{-12} \text{ F}$$

$$Z_i(f) := \left( \frac{1}{R_g} + 2j \cdot \pi \cdot f \cdot C_i \right)^{-1}$$

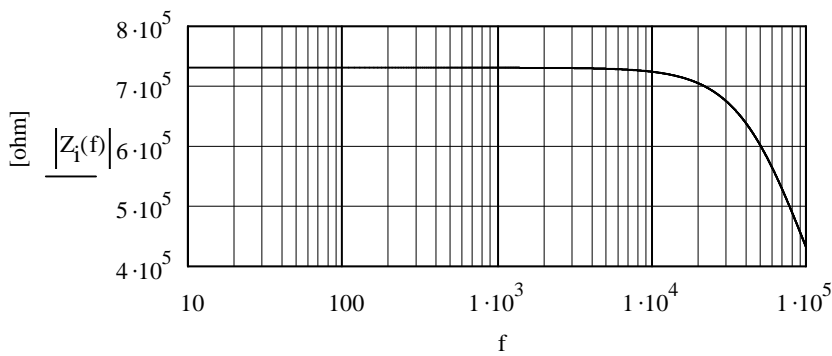


Fig. 10.12 Input impedance vs. frequency

$$R_L := 10^3 \Omega, 1.5 \cdot 10^3 \Omega .. 100 \cdot 10^3 \Omega$$

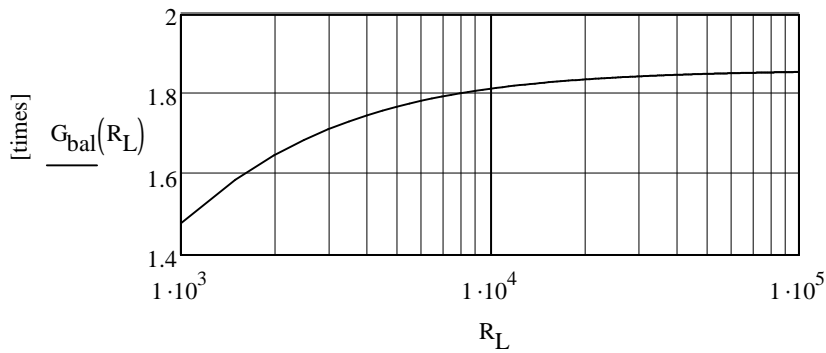


Fig. 10.13 Gain of the un-balanced<sup>[ohm]</sup> balanced converter PCS vs. balanced output load

$$R_{o, bal}(R_L) := R_L \cdot \left( \frac{G_{0, bal}}{G_{bal}(R_L)} - 1 \right)$$

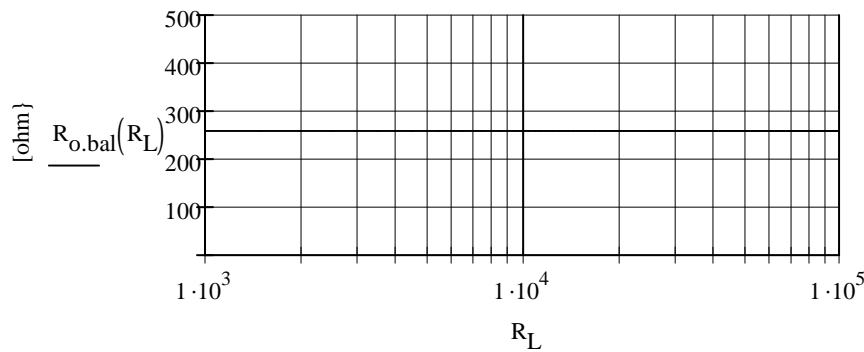


Fig. 10.14 Output resistance of the balanced output vs. balanced output load

#### 1.4 Equal capacitances parallel to $R = R_a = R_c$

$$C = C_a = C_c \quad \Rightarrow \quad Z_a(f) = Z_c(f) = Z(f) \quad R_L := 7.8 \cdot 10^6 \Omega$$

$$C_1 := 1 \cdot 10^{-9} \text{ F} \quad C_2 := 10 \cdot 10^{-9} \text{ F} \quad C_3 := 33 \cdot 10^{-9} \text{ F} \quad C_4 := 100 \cdot 10^{-9} \text{ F}$$

$$Z_1(f) := \left( \frac{1}{R} + 2j \cdot \pi \cdot f \cdot C_1 \right)^{-1} \quad Z_2(f) := \left( \frac{1}{R} + 2j \cdot \pi \cdot f \cdot C_2 \right)^{-1} \quad Z_3(f) := \left( \frac{1}{R} + 2j \cdot \pi \cdot f \cdot C_3 \right)^{-1} \quad Z_4(f) := \left( \frac{1}{R} + 2j \cdot \pi \cdot f \cdot C_4 \right)^{-1}$$

$$\Rightarrow G_{bal1}(f, R_L) := \frac{2 \cdot \mu}{2 + \mu + r_a \cdot \left( \frac{1}{Z_1(f)} + \frac{1}{0.5 \cdot R_L} \right)} \quad G_{bal2}(f, R_L) := \frac{2 \cdot \mu}{2 + \mu + r_a \cdot \left( \frac{1}{Z_2(f)} + \frac{1}{0.5 \cdot R_L} \right)}$$

$$G_{bal3}(f, R_L) := \frac{2 \cdot \mu}{2 + \mu + r_a \cdot \left( \frac{1}{Z_3(f)} + \frac{1}{0.5 \cdot R_L} \right)}$$

$$G_{bal4}(f, R_L) := \frac{2 \cdot \mu}{2 + \mu + r_a \cdot \left( \frac{1}{Z_4(f)} + \frac{1}{0.5 \cdot R_L} \right)}$$

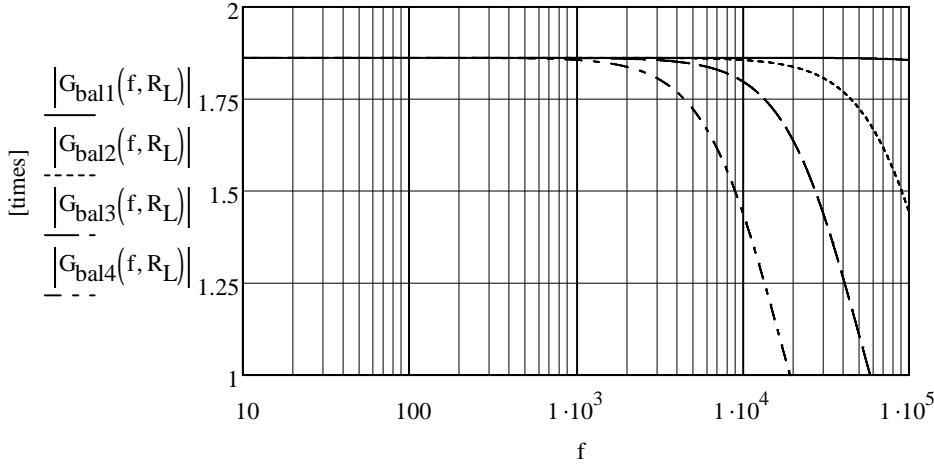


Fig. 10.15 Balanced gain vs. frequency with equal additional capacitances parallel to the anode and cathode load resistors R

$$k := 1..5$$

$$f := 20 \cdot 10^3 \text{ Hz}$$

$$C_{pk} :=$$

$10 \cdot 10^{-12} \text{ F}$
$1 \cdot 10^{-9} \text{ F}$
$10 \cdot 10^{-9} \text{ F}$
$33 \cdot 10^{-9} \text{ F}$
$100 \cdot 10^{-9} \text{ F}$

$$Z_k := \left( \frac{1}{R} + 2j \cdot \pi \cdot f \cdot C_{pk} \right)^{-1}$$

$$G_{bal_k} := \frac{2 \cdot \mu}{2 + \mu + r_a \cdot \left( \frac{1}{Z_k} + \frac{1}{0.5 \cdot R_L} \right)}$$

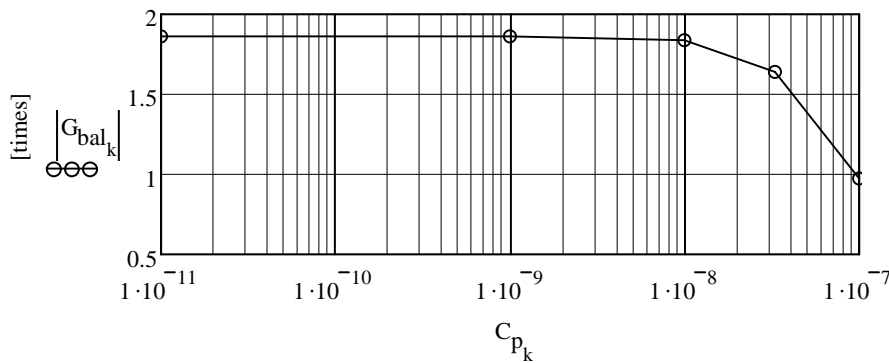


Fig. 10.15 Balanced gain at  $f = 20 \text{ kHz}$  vs. various equal additional capacitances parallel to the anode and cathode load resistors R

## 2. CPS used as un-balanced to un-balanced converter via anode OR cathode output

### 2.1 Idle gains

via the anode alone:  $G_{0,a} := -\mu \cdot \frac{R_a}{r_a + R_a + (1 + \mu) \cdot R_c}$   $G_{0,a} = -931.293 \times 10^{-3}$

via the cathode alone:  $G_{0,c} := \mu \cdot \frac{R_c}{r_a + R_a + (1 + \mu) \cdot R_c}$   $G_{0,c} = 931.293 \times 10^{-3}$

### 2.2 Output resistances (between respective output and ground!)

via the anode alone:  $R_{o,a} := \frac{R_a \cdot [r_a + (1 + \mu) \cdot R_c]}{r_a + R_a + (1 + \mu) \cdot R_c}$   $R_{o,a} = 14.549 \times 10^3 \Omega$

via the cathode alone:  $r_c := \frac{r_a + R_a}{1 + \mu}$   $R_{o,c} := \frac{R_c \cdot r_c}{r_c + R_c}$   $R_{o,c} = 579.972 \times 10^0 \Omega$

### 2.3 Output loaded gains (outputs separately loaded!)

$R_{L,a} := 5 \cdot 10^3 \Omega$   $R_{L,c} := 5 \cdot 10^3 \Omega$

$G_a(R_{L,a}) := G_{0,a} \cdot \frac{R_{L,a}}{R_{L,a} + R_{o,a}}$   $G_a(R_{L,a}) = -238.19 \times 10^{-3}$

$G_c(R_{L,c}) := G_{0,c} \cdot \frac{R_{L,c}}{R_{L,c} + R_{o,c}}$   $G_c(R_{L,c}) = 885.48 \times 10^{-3}$



3. Derivation of the balanced equations and proof of the above given ones

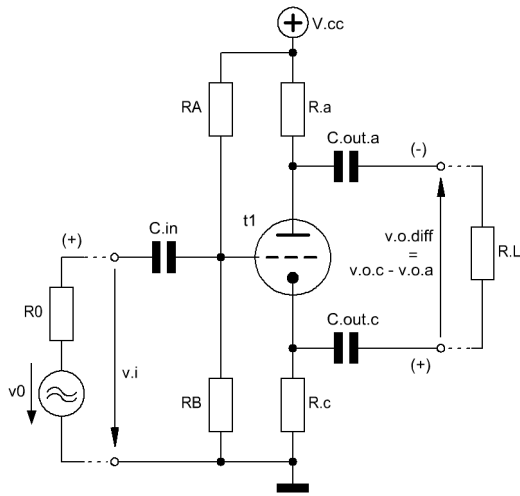


Fig. 10.16 Un-balanced to balanced converter

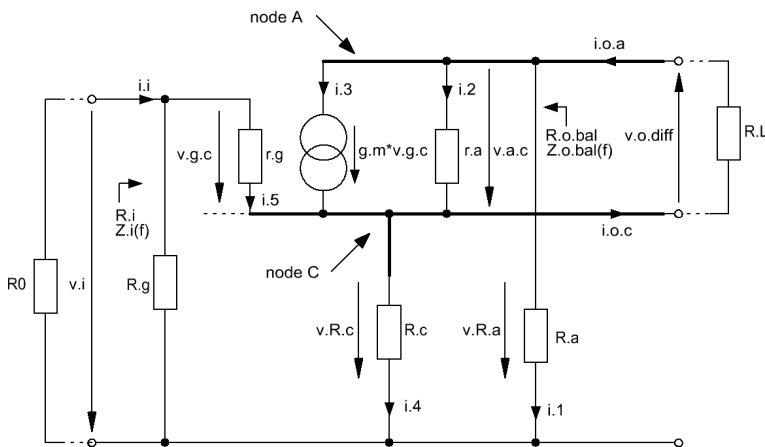


Fig. 10.17 Equivalent circuit of Fig. 10.16

3.1 Relevant derivation equations

node A:  $i_1 + i_2 + i_3 = i_{o.a}$

node C:  $i_2 + i_3 = i_{o.c} + i_4$        $i_{o.a} = i_{o.c} \Rightarrow i_1 + i_2 + i_3 = i_2 + i_3 - i_4 \Rightarrow i_1 = -i_4$

$R_a = R_c = R \Rightarrow v_{R.c} = -v_{R.a}$

$i_1 = \frac{v_{R.a}}{R}$        $i_2 = \frac{v_{a.c}}{r_a}$        $i_3 = g_m \cdot v_{g.c}$        $i_4 = \frac{v_{R.c}}{R}$        $i_{o.c} = i_{o.a} = \frac{v_{o.diff}}{R_L}$

$v_{o.diff} = -v_{a.c}$        $v_{g.c} = v_i - v_{R.c}$        $v_{R.c} + v_{a.c} = v_{R.a}$        $v_{a.c} = v_{R.a} - v_{R.c} = -v_{o.diff} = -2 \cdot v_{R.c}$        $v_{R.c} = \frac{v_{o.diff}}{2}$

$$\Rightarrow \frac{v_{R.a}}{R} + \frac{v_{a.c}}{r_a} + g_m \cdot v_{gc} = \frac{v_{o.diff}}{R_L}$$

$$\Rightarrow \frac{v_{a.c}}{r_a} + g_m \cdot v_{gc} = \frac{v_{o.diff}}{R_L} + \frac{v_{R.c}}{R}$$

### 3.2 Derivation of the differential (= balanced) gain with output loaded (see Fig. 10.17)

$$\Rightarrow \frac{-v_{o.diff}}{r_a} + g_m \cdot v_i - g_m \cdot \frac{v_{o.diff}}{2} = \frac{v_{o.diff}}{R_L} + \frac{v_{o.diff}}{2 \cdot R}$$

$$v_{o.diff} \cdot \left( -\frac{1}{r_a} - \frac{g_m}{2} - \frac{1}{R_L} - \frac{1}{2 \cdot R} \right) = -v_i \cdot g_m \Rightarrow \frac{v_{o.diff}}{v_i} = G_{diff}(R_L) = -g_m \cdot \left( -\frac{1}{r_a} - \frac{g_m}{2} - \frac{1}{R_L} - \frac{1}{2 \cdot R} \right)^{-1}$$

$$\frac{v_{o.diff}}{v_i} = G_{diff}(R_L) = \frac{R \cdot 2 \cdot g_m \cdot r_a \cdot R_L}{2 \cdot R_L \cdot R + g_m \cdot r_a \cdot R_L \cdot R + 2 \cdot r_a \cdot R + r_a \cdot R_L}$$

$$R := 15 \cdot 10^3 \Omega$$

$$R_L := 10 \cdot 10^3 \Omega$$

$$\frac{R \cdot 2 \cdot g_m \cdot r_a \cdot R_L}{2 \cdot R_L \cdot R + g_m \cdot r_a \cdot R_L \cdot R + 2 \cdot r_a \cdot R + r_a \cdot R_L} = 1.816 \times 10^0$$

$$G_{diff1}(R_L) := \frac{2 \cdot \mu \cdot R \cdot R_L}{(2 + \mu) \cdot (R_L \cdot R) + r_a \cdot (2 \cdot R + R_L)}$$

$$G_{diff1}(R_L) = 1.816 \times 10^0$$

$$\Rightarrow G_{diff}(R_L) := \frac{2 \cdot \mu}{2 + \mu + r_a \cdot \left( \frac{1}{R} + \frac{1}{0.5 \cdot R_L} \right)}$$

$$G_{diff}(R_L) = 1.816 \times 10^0$$

$$\Rightarrow G_{diff}(R_L) = G_{bal}(R_L)$$

**q.e.d**

with  $R_L = \text{infinite}$ :

$$G_{0.diff} := \frac{2 \cdot \mu}{(2 + \mu) + \frac{r_a}{R}}$$

$$G_{0.diff} = 1.863 \times 10^0$$

$$\Rightarrow G_{0.diff} = G_{0.bal}$$

**q.e.d**

### 3.3 Derivation of the differential (= balanced) output resistance (see Fig. 10.17)

#### 3.3.1 Equations approach

$$i_{o.a} = i_1 + i_2 + i_3 \quad v_{o.diff} = -i_2 \cdot r_a \quad i_2 = \frac{-v_{o.diff}}{r_a} \quad i_3 = g_m \cdot v_{g.c} \quad i_1 = \frac{v_{R.a}}{R}$$

$$i_{o.a} = \frac{v_{R.a}}{R} - \frac{v_{o.diff}}{r_a} + g_m \cdot v_{g.c} = \frac{-v_{o.diff}}{2 \cdot R} - \frac{v_{o.diff}}{r_a} + g_m \cdot v_i - \frac{g_m}{2} \cdot v_{o.diff}$$

with  $v_i = 0 \Rightarrow$

$$i_{o.a} = v_{o.diff} \cdot \left( -\frac{1}{2 \cdot R} - \frac{1}{r_a} - \frac{g_m}{2} \right)$$

$$R_{o.diff} = \frac{-v_{o.diff}}{i_{o.a}} = \frac{-v_{o.diff}}{i_{o.c}} = \frac{-v_{o.diff}}{v_{o.diff} \cdot \left( -\frac{1}{2 \cdot R} - \frac{1}{r_a} - \frac{g_m}{2} \right)} = \frac{1}{\frac{1}{2 \cdot R} + \frac{1}{r_a} + \frac{g_m}{2}}$$

$$R_{o.diff1} := \frac{1}{\frac{1}{2 \cdot R} + \frac{g_m}{2} + \frac{1}{r_a}} \quad R_{o.diff1} = 258.693 \times 10^0 \Omega$$

$$\Rightarrow R_{o.diff} := \frac{2 \cdot r_a \cdot R}{r_a + (2 + \mu) \cdot R} \quad R_{o.diff} = 258.693 \times 10^0 \Omega$$

$$\Rightarrow R_{o.diff} = R_{o.bal} \quad \mathbf{q.e.d}$$

#### 3.3.2 '0.5-times' approach

At the gain  $G_{bal,L} = 0.5 \cdot G_{bal,nL}$  the output resistance  $R_{o,bal}$  equals the load resistance  $R_L$ . Hence,

$$0.5 = \frac{G_{bal}(R_L)}{G_{0,bal}} \Rightarrow 0.5 = \frac{\frac{2 \cdot \mu}{2 + \mu + r_a \cdot \left( \frac{1}{R} + \frac{1}{0.5 \cdot R_L} \right)}}{\frac{2 \cdot \mu}{(2 + \mu) + \frac{r_a}{R}}}$$

$$\Rightarrow R_L := \frac{2 \cdot r_a \cdot R}{r_a + (2 + \mu) \cdot R} \Rightarrow R_L = 258.693 \times 10^0 \Omega$$

with  $R_{o,bal} := R_L \Rightarrow R_{o,bal} = 258.693 \times 10^0 \Omega \quad \mathbf{q.e.d}$